

MC13783 Buck and Boost Inductor Sizing

by: Power Management Application Team

1 Introduction

The purpose of this application note is to provide a method of choosing the size of the inductors for the optimized switching regulators versus the current consumption of the application. This will allow to optimize the size and the cost of these components.

The recommendations for external components used for a reference or application design implemented with the MC13783 are outlined in the application note *External Component Recommendations for the MC13783 Reference Design* (document number: AN3295).

2 Buck Converter

The buck converter architecture used for the MC13783 is a simple PWM voltage mode control topology using a clock, which is 32 times the crystal oscillator clock of 1.024 MHz. Pulse skip mode is supported and would occur at a current level determined by the external L,C components and the input and output levels.

Contents

1 Introduction	1
2 Buck Converter	1
3 Boost Converter	4

2.1 Current Limit

The current limit value not only is temperature-and process-dependent, but it is also related to the slope of the current flowing through the power switch (this includes notion of delay). The current limit tolerance is 800-1000 mA for single connection and is 1300-1500 mA for parallel connection.

2.2 Theoretical Inductor Sizing

For a buck topology switching power supply as shown in Figure 1, the external components selection is driven by input, output voltage levels, load requirements, switching frequency and desired amount of voltage output ripple (ripple current).

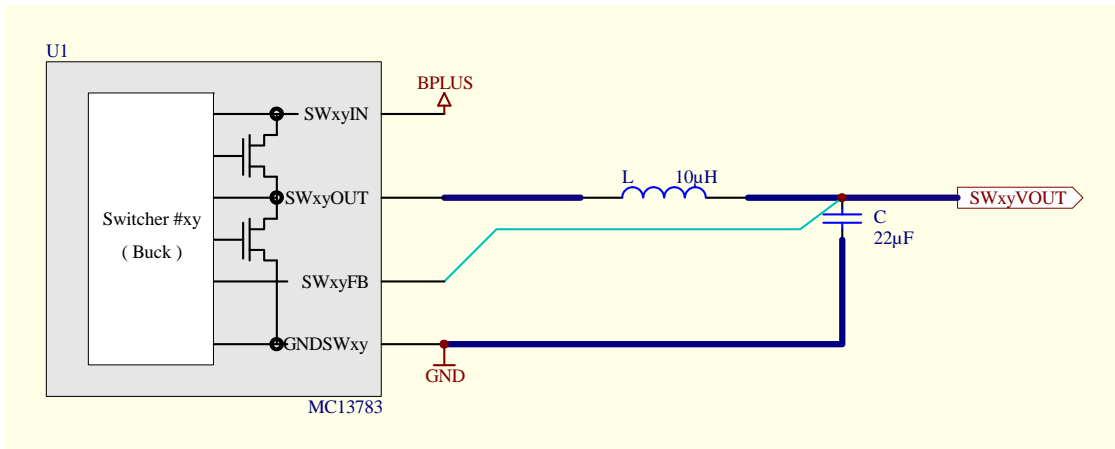


Figure 1. MC13783 Buck Converter Topology for Single Connection

The operating frequency and inductor selection are inter-related in that higher operating frequencies allow the use of a smaller inductor value. However, operating at a higher frequency generally results in lower efficiency because of increased internal gate charge losses.

For a given switching frequency, the highest inductor current ripple occurs at maximum input voltage and maximum output voltage. The following equations are presented for L sizing.

$$\Delta I_{L_{max}} = \frac{1}{f_s \cdot L} \cdot V_{out_{max}} \cdot \left(1 - \frac{V_{out_{max}}}{V_{in_{max}}} \right)$$

Eqn. 1

However, the inductor current ripple is directly proportional to the amount of voltage output ripple. All DC current of the inductor is provided to the load and the remaining AC current is going through the output capacitor.

$$I_{L_{ac}} = I_{C_{ac}}$$

Eqn. 2

In most cases when ESR is large enough, the maximum output voltage ripple is given by [Equation 3](#):

$$\Delta V_{out} = ESR \cdot \Delta I_L$$

Eqn. 3

Accepting the larger values of inductor current ripple allows the use of lower inductance, but results in higher output voltage ripple and greater core and power device conduction losses.

$$L = \frac{1}{f_s \cdot \Delta I_{Lmax}} \cdot V_{outmax} \cdot \left(1 - \frac{V_{outmax}}{V_{inmax}}\right)$$

Eqn. 4

All conduction losses are proportional to the RMS inductor current as shown in [Equation 5](#):

$$\text{ConductionLOSSES} \sim I_{Lrms}^2 = I_L^2 + \frac{\Delta I_L^2}{12}$$

Eqn. 5

Most of the time the inductor will be selected to reach the required output voltage ripple, especially when the DC-DC converter will directly supply the IC without the "filtering" of the low drop out linear regulators. Its value will result from the following equation:

$$L = \frac{ESR}{f_s \cdot \Delta V_{outmax}} \cdot V_{outmax} \cdot \left(1 - \frac{V_{outmax}}{V_{inmax}}\right)$$

Eqn. 6

Physical size of the inductor is roughly proportional to its peak energy storage as shown in [Equation 7](#).

$$E = \frac{1}{2} \cdot L \cdot I_{peak}^2$$

$$I_{Lpeak} = I_{Ldc} + \frac{\Delta I_L}{2}$$

$$I_{Lpeakmax} = I_{Ldcmax} + \frac{1}{f_s \cdot L} \cdot V_{outmax} \cdot \left(1 - \frac{V_{outmax}}{V_{inmax}}\right)$$

Eqn. 7

The $I_{Lpeak_{max}}$ is the maximum inductor peak current in steady state operation. During transient (especially at power-up), the peak current can be higher since the power device can be turned on during $T_{on_{max}}$ for more than one cycle. In this case, the peak current will be limited by the current limit function.

2.3 Numerical Application Example

A numerical application example of the MC13783 is if a switcher is used with a 750 mA max. DC load, a 1.6 V max. output voltage, and 4.2 V maximum input voltage, then:

$$L = 10 \mu\text{H}$$

$$F_s = 1.024 \text{ MHz}$$

$$I_{\text{peak}_{\text{max}}} = 750 \text{ mA} + 96 \text{ mA} = 846 \text{ mA}$$

3 Boost Converter

The boost converter architecture used for the MC13783 is a simple PWM current mode control topology using a clock which is 32 times the crystal oscillator clock (1.024 MHz). Pulse skip mode is supported and would occur at a current level determined by the external L,C components and the input and output levels.

3.1 Theoretical Inductor Sizing

For a boost topology switching power supply as shown in Figure 2, the external components selection is driven by input, output voltages levels, load requirements, switching frequency, and desired amount of voltage output ripple (ripple current).

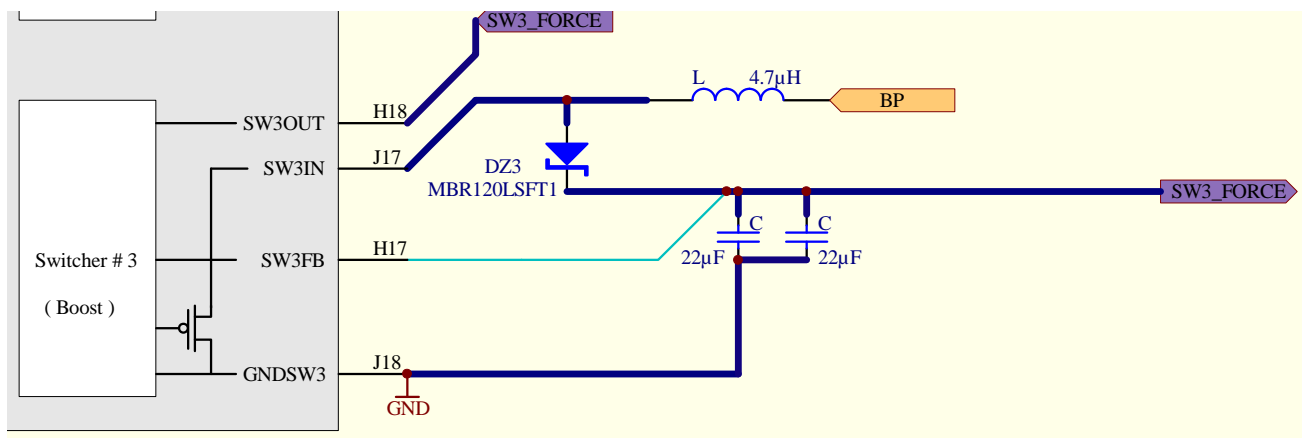


Figure 2. MC13783 Boost Converter Topology

The operating frequency and inductor selection are inter-related in that higher operating frequencies allow the use of smaller inductor value. However, operating at a higher frequency generally results in lower efficiency because of increased internal gate charge losses. For a given switching frequency, the highest inductor current ripple occurs at maximum output voltage and for $V_{in} = V_{out}/2$.

$$\Delta I_L = \frac{1}{f_s \cdot L} \cdot V_{in} \cdot \left(1 - \frac{V_{in}}{V_{out}}\right)$$

$$\Delta I_{L_{max}} = \frac{1}{f_s \cdot L} \cdot \frac{V_{out_{max}}}{4}$$

Eqn. 8

Considering the following relation in [Equation 9](#).

$$\frac{V_{out}}{2} < V_{in}$$

Eqn. 9

However, the inductor current ripple is directly proportional the amount of voltage output ripple. When the power switch is closed, the current in the output capacitor is equaled to $(-I_{load})$, while when it is open as shown in [Equation 10](#).

$$I_C(t) = I_L(t) - I_{out}$$

$$I_{L_{ac}} = I_{C_{ac}}$$

Eqn. 10

In most cases when ESR is large enough and when the amount of capacitance is large enough such that the ripple can be ignored due to the capacitor, the maximum output voltage ripple is given by:

a) Discontinuous Conduction Mode:

$$\Delta V_{out} = ESR \cdot \Delta I_L$$

Eqn. 11

b) Continuous Conduction Mode:

$$\Delta V_{out} = ESR \cdot (\Delta I_L/2 + 4I_{load})$$

Accepting the larger values of inductor current ripple allows the use of lower inductance, but results in higher output voltage ripple and greater core and power device conduction losses.

$$L = \frac{1}{f_s \cdot \Delta I_{L_{max}}} \cdot \frac{V_{out_{max}}}{4}$$

Eqn. 12

All conduction losses are proportional to the RMS inductor current as shown in [Equation 13](#):

$$\text{Conduction LOSSES} \sim I_{L_{\text{rms}}}^2 = I_L^2 + \frac{\Delta I_L^2}{12}$$

Eqn. 13

Most of the time, the inductor will be chosen to reach the required output voltage ripple, especially when the DC-DC converter will directly supply the IC without "filtering" of the low drop out linear regulators. Its value will result from the following equation:

$$L = \frac{\text{ESR}}{f_s \cdot \Delta V_{\text{outmax}}} \cdot \frac{V_{\text{outmax}}}{4}$$

Eqn. 14

Physical size of the inductor is roughly proportional to its peak energy storage.

$$E = \frac{1}{2} \cdot L \cdot I_{\text{peak}}^2$$

$$I_{L_{\text{peak}}} = I_{L_{\text{dc}}} + \frac{\Delta I_L}{2}$$

$$I_{L_{\text{peak}}} = \frac{I_{\text{outmax}}}{1-D} + \frac{1}{f_s \cdot L \cdot 2} \cdot V_{\text{in}} \cdot \left(1 - \frac{V_{\text{in}}}{V_{\text{out}}}\right)$$

$$I_{L_{\text{peak}}} = \frac{V_{\text{out}}}{V_{\text{in}}} \cdot I_{\text{out}} + \frac{1}{f_s \cdot L \cdot 2} \cdot V_{\text{in}} \cdot \left(1 - \frac{V_{\text{in}}}{V_{\text{out}}}\right)$$

$$I_{L_{\text{peakmax}}} = \frac{V_{\text{outmax}}}{V_{\text{inmin}}} \cdot I_{\text{outmax}} + \frac{1}{f_s \cdot L \cdot 2} \cdot V_{\text{inmin}} \cdot \left(1 - \frac{V_{\text{inmin}}}{V_{\text{outmax}}}\right)$$

Eqn. 15

The $I_{L_{\text{peakmax}}}$ is the maximum inductor peak current in steady state operation. During transient (especially at power-up), the peak current can be higher since the power device can be turned on during T_{onmax} for more than one cycle. In this case, the peak current will be limited by the current limit function.

3.2 Numerical Application Example

A numerical application example of the MC13783 is if a switcher used with a 200 mA max. DC load, a 5.5 V max. output voltage, and 3.05 V minimum input voltage, then:

$$L = 4.7 \mu\text{H}$$

$$f_s = 1.024 \text{ MHz}$$

$$I_{L_{\text{peakmax}}} = 360 \text{ mA} + 140 \text{ mA} = 500 \text{ mA}$$

NOTES

How to Reach Us:

Home Page:

www.freescale.com

Web Support:

<http://www.freescale.com/support>

USA/Europe or Locations Not Listed:

Freescale Semiconductor, Inc.
Technical Information Center, EL516
2100 East Elliot Road
Tempe, Arizona 85284
1-800-521-6274 or +1-480-768-2130
www.freescale.com/support

Europe, Middle East, and Africa:

Freescale Halbleiter Deutschland GmbH
Technical Information Center
Schatzbogen 7
81829 Muenchen, Germany
+44 1296 380 456 (English)
+46 8 52200080 (English)
+49 89 92103 559 (German)
+33 1 69 35 48 48 (French)
www.freescale.com/support

Japan:

Freescale Semiconductor Japan Ltd.
Headquarters
ARCO Tower 15F
1-8-1, Shimo-Meguro, Meguro-ku,
Tokyo 153-0064
Japan
0120 191014 or +81 3 5437 9125
support.japan@freescale.com

Asia/Pacific:

Freescale Semiconductor China Ltd.
Exchange Building 23F
No. 118 Jianguo Road
Chaoyang District
Beijing 100022
China
+86 10 5879 8000
support.asia@freescale.com

For Literature Requests Only:

Freescale Semiconductor Literature Distribution Center
1-800-441-2447 or +1-303-675-2140
Fax: +1-303-675-2150
LDCForFreescaleSemiconductor@hibbertgroup.com

Information in this document is provided solely to enable system and software implementers to use Freescale Semiconductor products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits or integrated circuits based on the information in this document.

Freescale Semiconductor reserves the right to make changes without further notice to any products herein. Freescale Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Freescale Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters that may be provided in Freescale Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals", must be validated for each customer application by customer's technical experts. Freescale Semiconductor does not convey any license under its patent rights nor the rights of others. Freescale Semiconductor products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Freescale Semiconductor product could create a situation where personal injury or death may occur. Should Buyer purchase or use Freescale Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold Freescale Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Freescale Semiconductor was negligent regarding the design or manufacture of the part.

Freescale™ and the Freescale logo are trademarks of Freescale Semiconductor, Inc. All other product or service names are the property of their respective owners.

© Freescale Semiconductor, Inc. 2006-2010. All rights reserved.